



# Current

The current, which is Coulomb's per second, is simply


$$I = ei_e = en_eAv_d$$

$e$  is the charge of the electron

$n_e$  is the density of electrons

$A$  is the cross sectional area of the wire

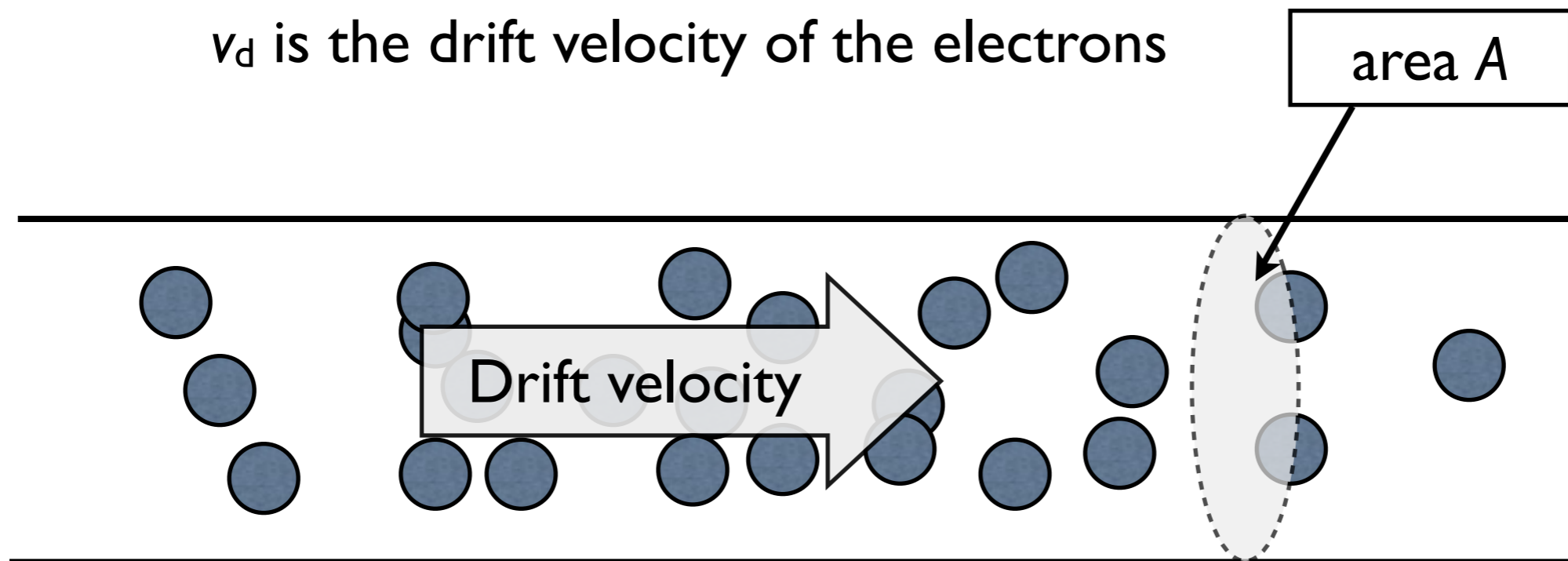$v_d$  is the drift velocity of the electrons



# Current and E-Field

Using the current from earlier, and the drift speed, the current is proportional to the electric field!

$$I = \frac{e^2 n_e \tau}{m_e} A E$$

which can be written as


$$I = \sigma A E \quad \text{where} \quad \sigma = \frac{e^2 n_e \tau}{m_e}$$

The **material constant  $\sigma$**  is called the **conductivity** (SI unit =  $\Omega^{-1} \text{ m}^{-1}$ ).

The **inverse quantity**  $\rho = \frac{1}{\sigma}$  is called the **resistivity** (SI unit:  $\Omega \text{ m}$ ).
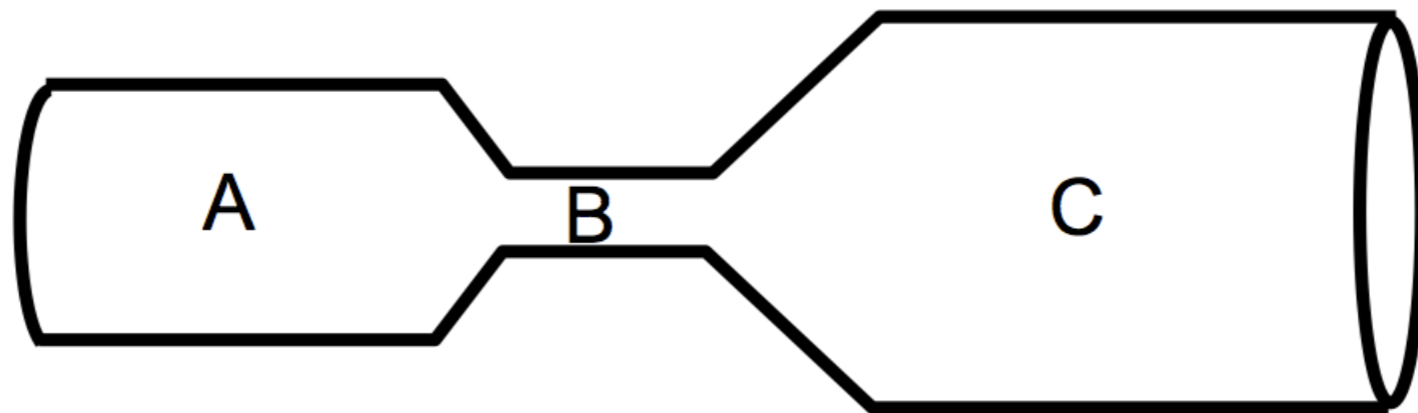
# Clicker Question

A copper cylinder is machined to have the following shape. The ends are connected to a battery so that a current flows through the copper.




Which region has the greatest magnitude of current,  $I$ ?

- a) A
- b) B
- c) C
- d) All three are the same
- e) Not sure/ not enough info
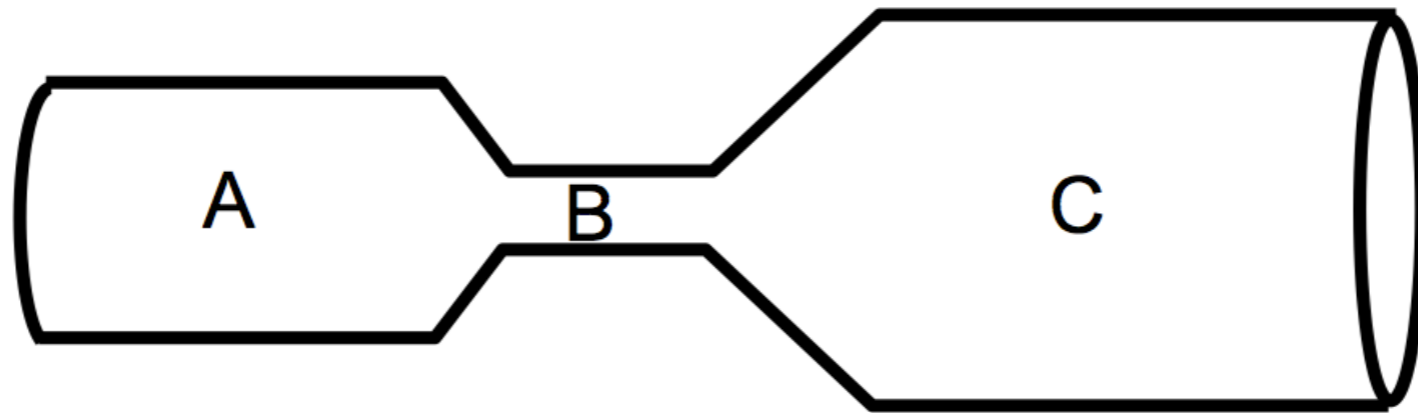
# Clicker Question

A copper cylinder is machined to have the following shape. The ends are connected to a battery so that a current flows through the copper.



Which region has the greatest magnitude of current,  $I$ ?

- a) A
- b) B
- c) C
- d) All three are the same
- e) Not sure/ not enough info


Current is conserved.  
Think of water flow.

# Current Density

The current divided by the cross sectional area gives us the current density,

$$J = \frac{I}{A} = \sigma E$$

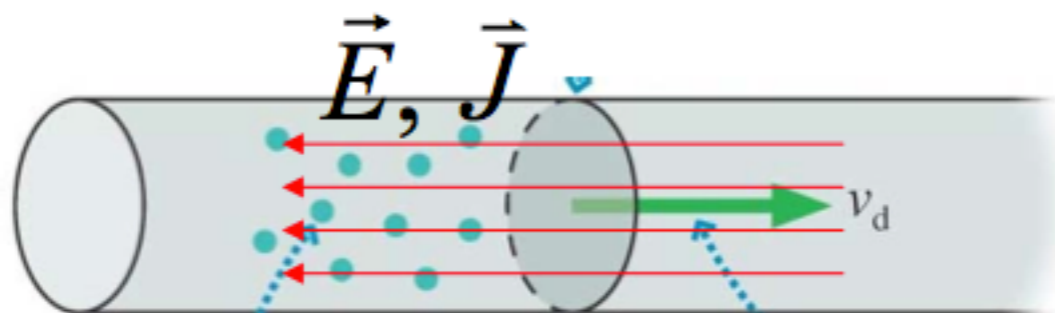
A **microscopic quantity** that is proportional to the **electric field**.



Note: The current actually flows against the electric field.
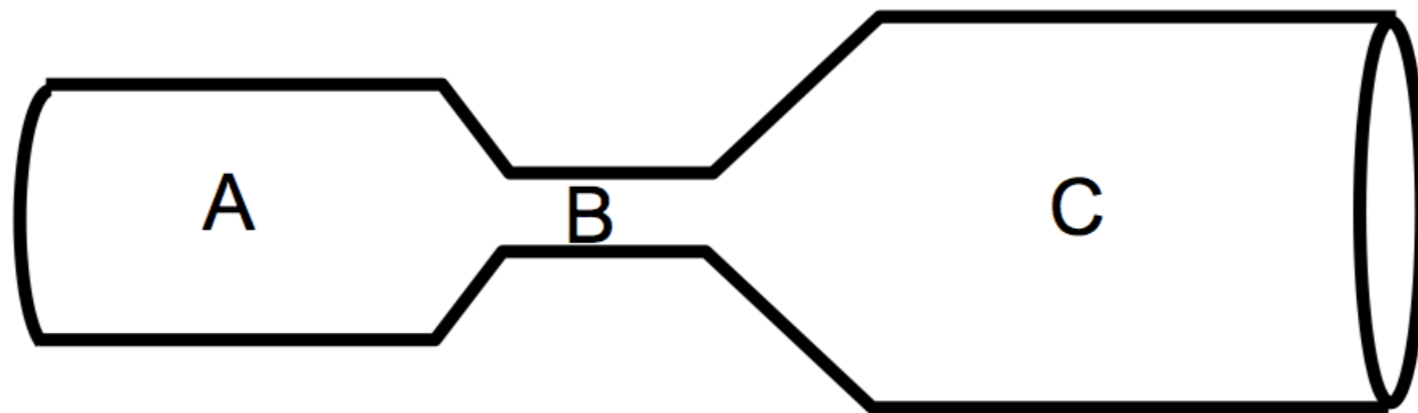
# Clicker Question

A copper cylinder is machined to have the following shape. The ends are connected to a battery so that a current flows through the copper.




Which region has the greatest current density  $|J|$ ?

- a) A
- b) B
- c) C
- d) All three are the same
- e) Not sure/ not enough info
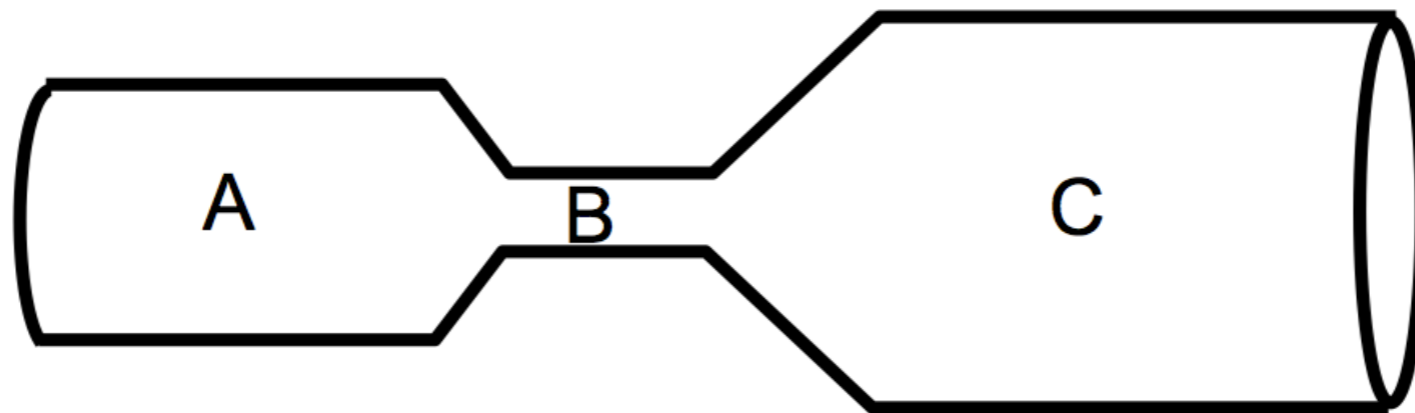
# Clicker Question

A copper cylinder is machined to have the following shape. The ends are connected to a battery so that a current flows through the copper.



Which region has the greatest current density  $|J|$ ?

- a) A
- b) B
- c) C
- d) All three are the same
- e) Not sure/ not enough info


Current is conserved so all the electrons must flow faster in the narrower part.

This also means that B has **greatest electric field** (question from PIAZZA)!


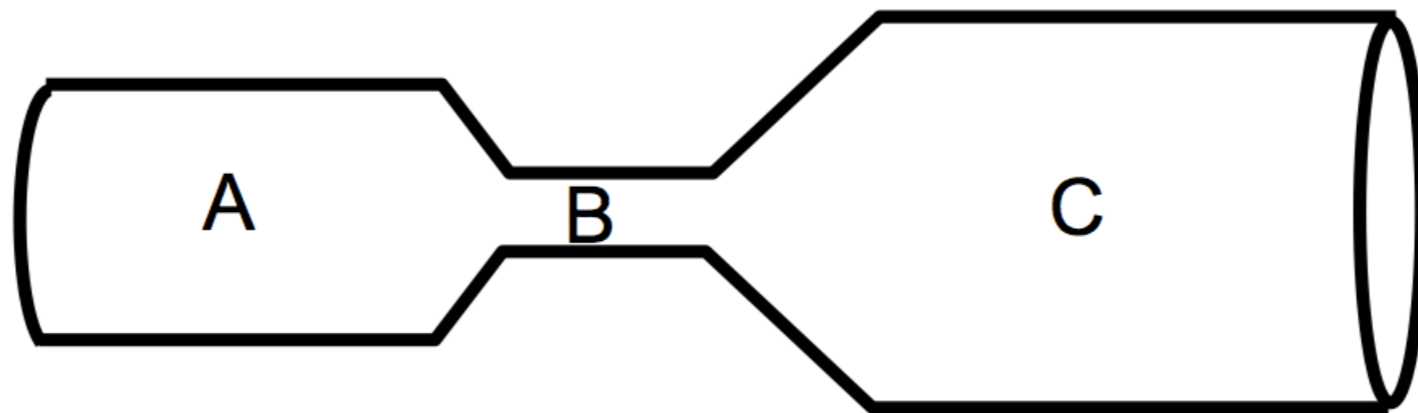
# Clicker Question

A copper cylinder is machined to have the following shape. The ends are connected to a battery so that a current flows through the copper.




Which region has the greatest conductivity  $\sigma$ ?

- a) A
- b) B
- c) C
- d) All three are the same
- e) Not sure/ not enough info
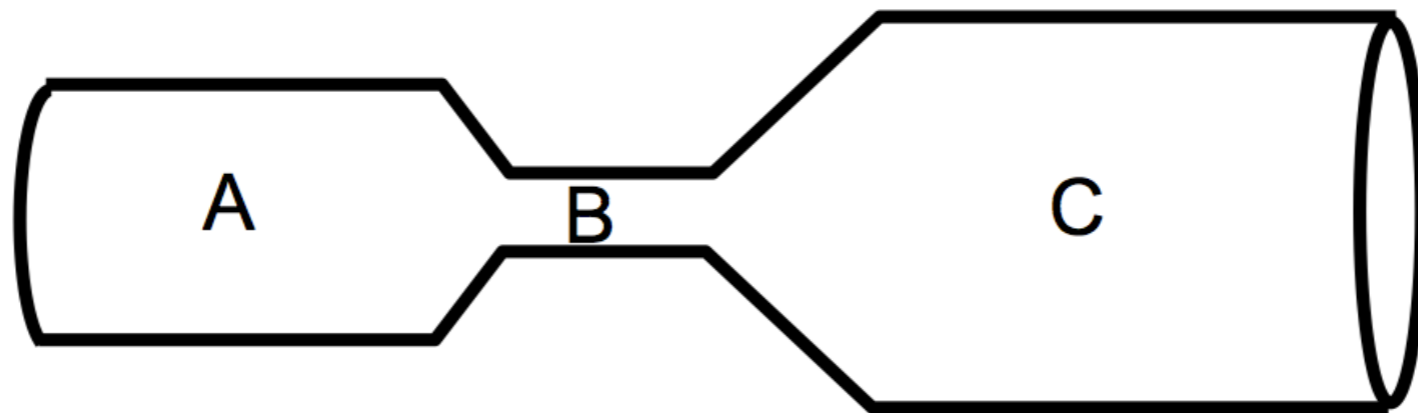
# Clicker Question

A copper cylinder is machined to have the following shape. The ends are connected to a battery so that a current flows through the copper.




Which region has the greatest conductivity  $\sigma$ ?

- a) A
- b) B
- c) C
- d) All three are the same
- e) Not sure/ not enough info

Conductivity and resistivity are microscopic properties of the material.
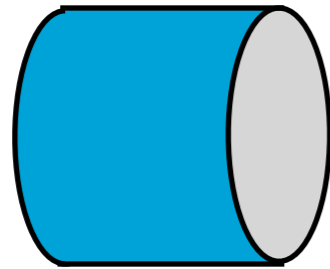
# Clicker Question

Rank these tubes by how hard it would be to push stuff (say towels) through them at the same rate.



A



B




C

- a) A harder than B harder than C
- b) C harder than B harder than A
- c) B harder than C harder than A
- d) A harder than C harder than B
- e) C harder than A harder than B
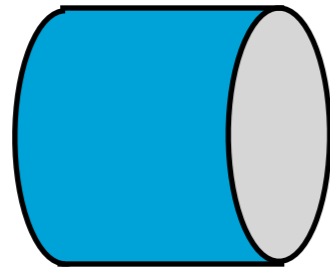
# Clicker Question

Rank these tubes by how hard it would be to push stuff (say towels) through them at the same rate.



A



B




C

- a) A harder than B harder than C
- b) C harder than B harder than A
- c) B harder than C harder than A
- d) A harder than C harder than B
- e) C harder than A harder than B

# Resistance and Resistivity

We can combine  $I = \sigma AE$  and  $V = Ed$  (but we're going to rename  $d$  to  $L$ ) to get

$$I = \sigma \frac{A}{L} V$$

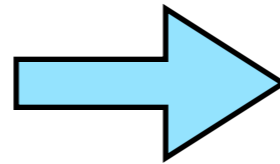


Ohm's Law !

$$\Delta V = IR$$


The resistance  $R$  of a real wire depends on the cross sectional area  $A$  and its length  $L$ :

$$R = \rho \frac{L}{A}$$

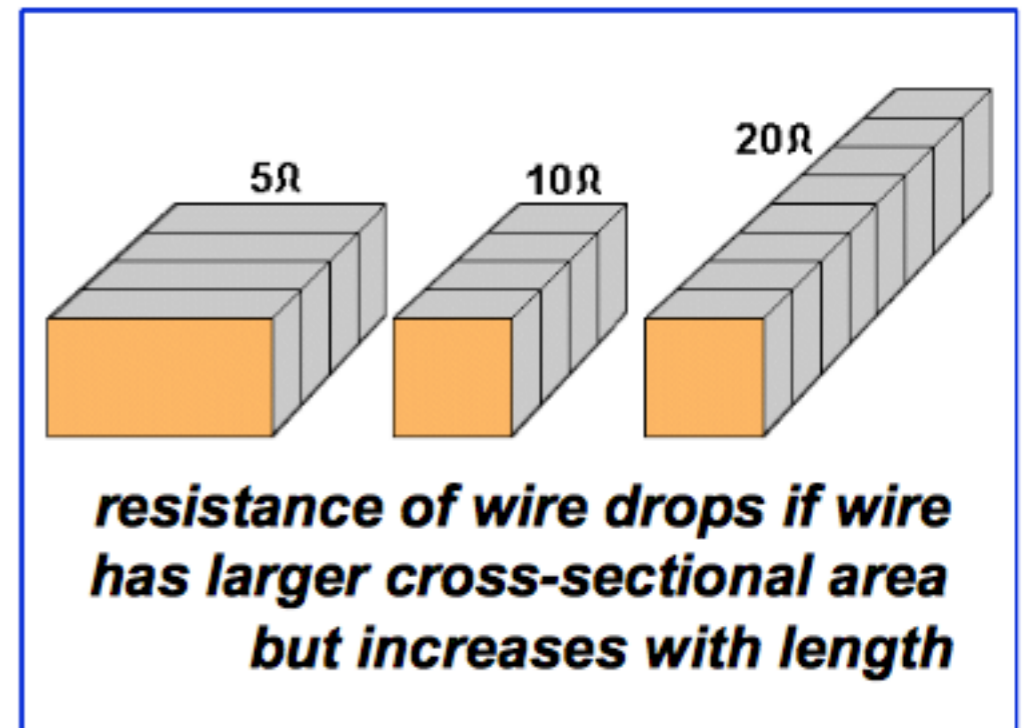A **macroscopic** property of the whole wire depending on the length and cross sectional area.



# Resistance

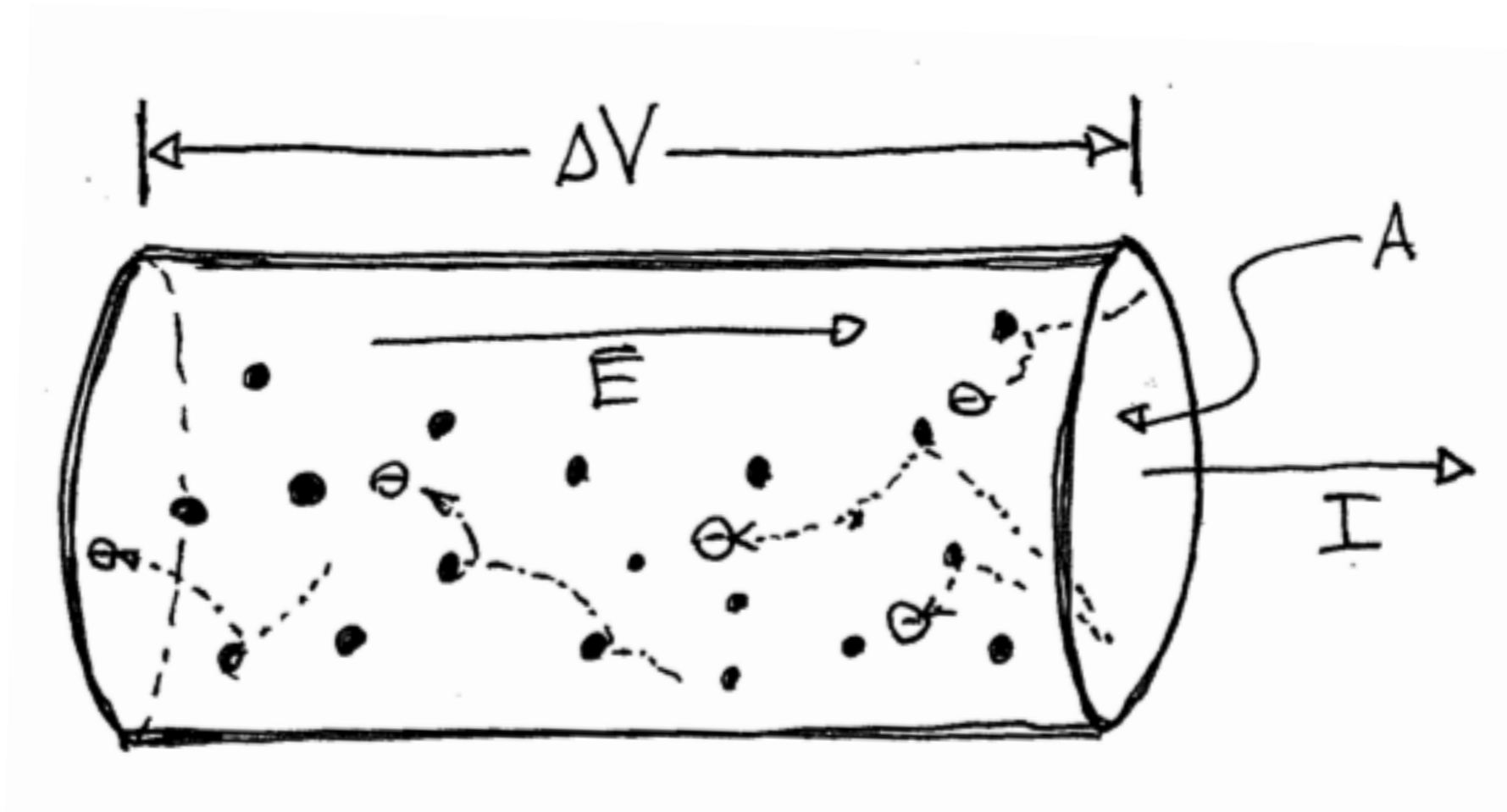

**Higher voltage leads to a larger electric field and an increase in drift speed and an increase in current.**

This leads to more collisions, more vibrations, and more energy loss (heat, light).

Battery Resistor Circuit

# Power Dissipated in a Resistor

The **drop in voltage across a resistor** means that energy is being lost:

$$\Delta U = q\Delta V$$


The **rate of energy lost** is the power:

$$P = \frac{dU}{dt} = \frac{dq}{dt}\Delta V = I\Delta V$$


Using Ohm's Law:

$$P = I^2 R = \frac{V^2}{R}$$

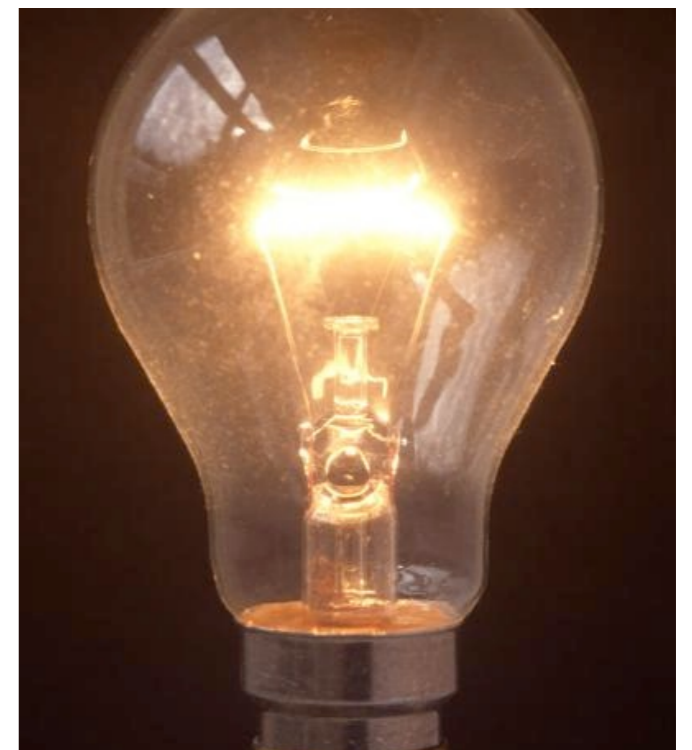This is the power dissipated in a component with resistance  $R$  and current  $I$  flowing through it.



# Circuit Analysis

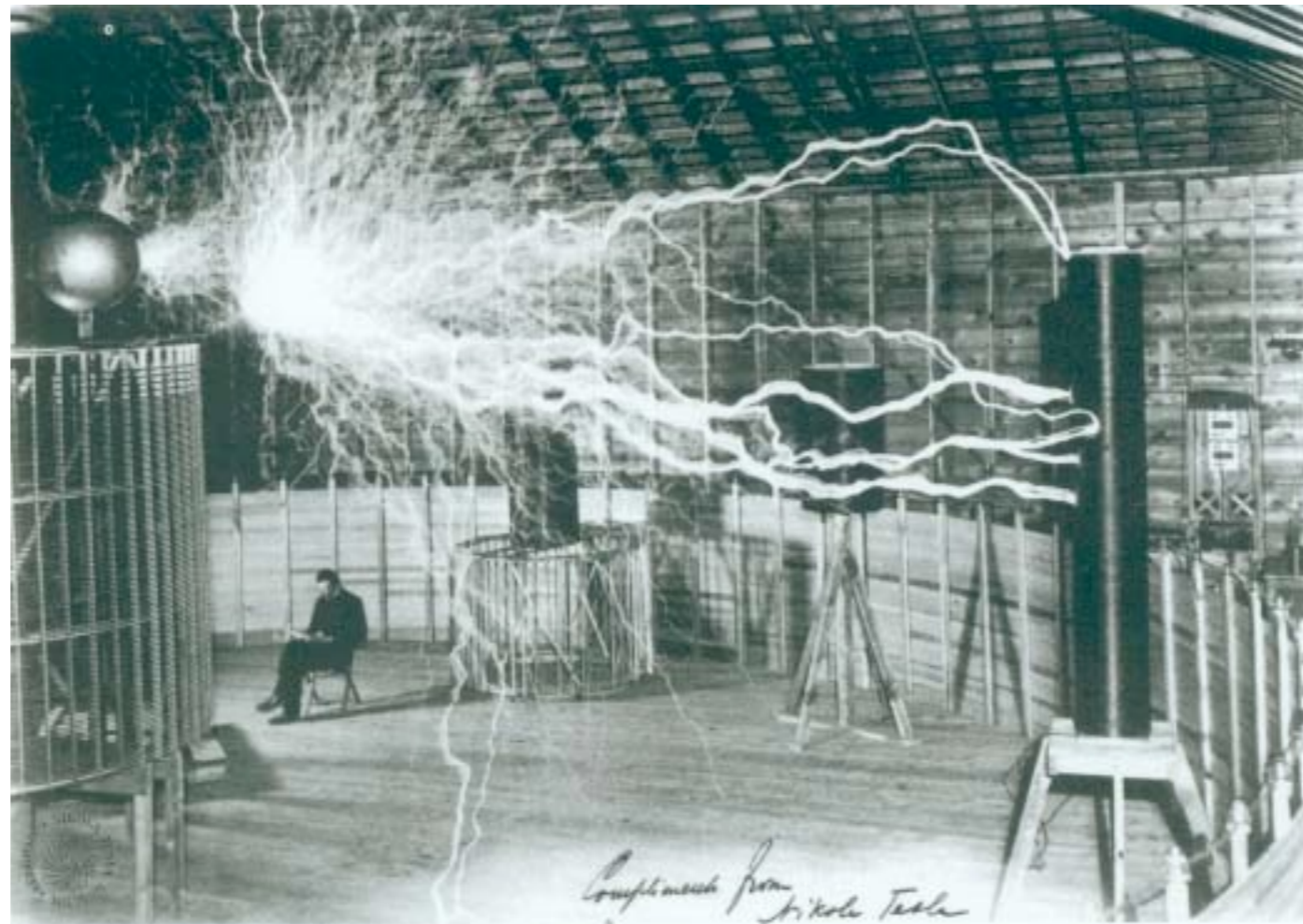



**Circuits Galore**  
**Problems 1 and 2**

# Kirchhoff's Loop law

A foundation of circuit analysis.

The loop law comes from path independence:


$$\Delta U = - \oint \vec{F} \cdot d\vec{s} = -q \oint \vec{E} \cdot d\vec{s} = 0$$

The change in energy around a closed path is zero.

We then know that  $U = qV$  gives

$$\Delta V_{\text{loop}} = 0$$


Which is the loop law.

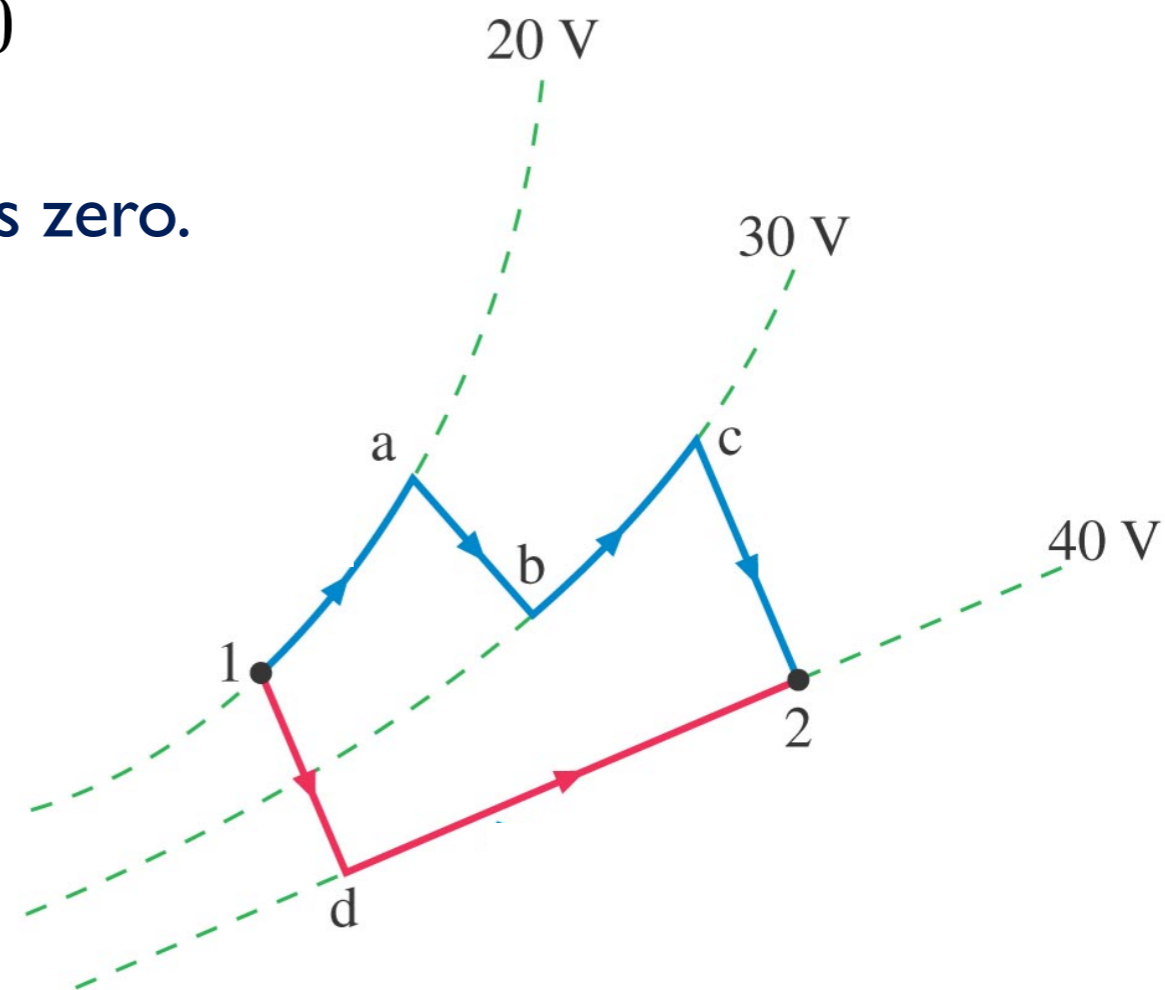


# Kirchhoff's Laws

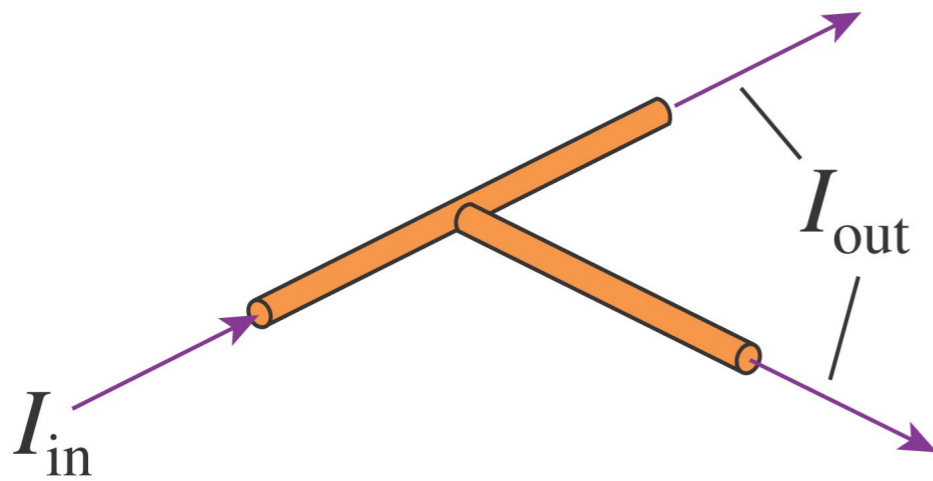**Kirchhoff's Laws are summarized as:**

$$\sum I_{in} = \sum I_{out} \text{ at a junction}$$



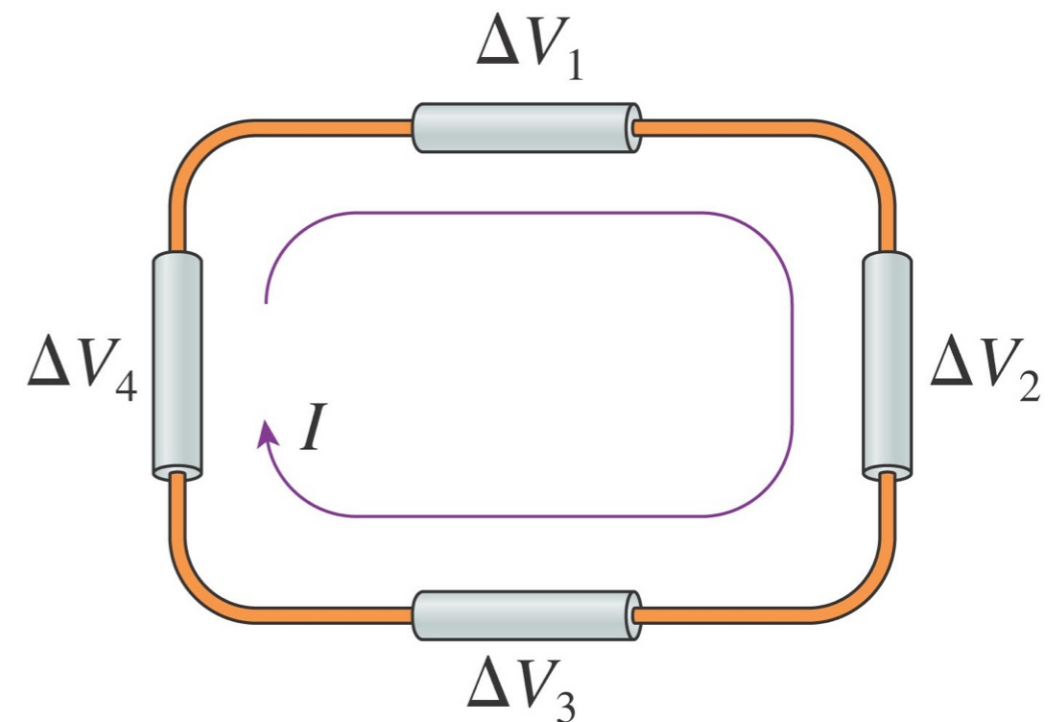
$$\sum_i \Delta V_i = 0 \quad \text{around closed loop}$$



$$\Delta V_1 + \Delta V_2 + \Delta V_3 + \Delta V_4 = 0$$

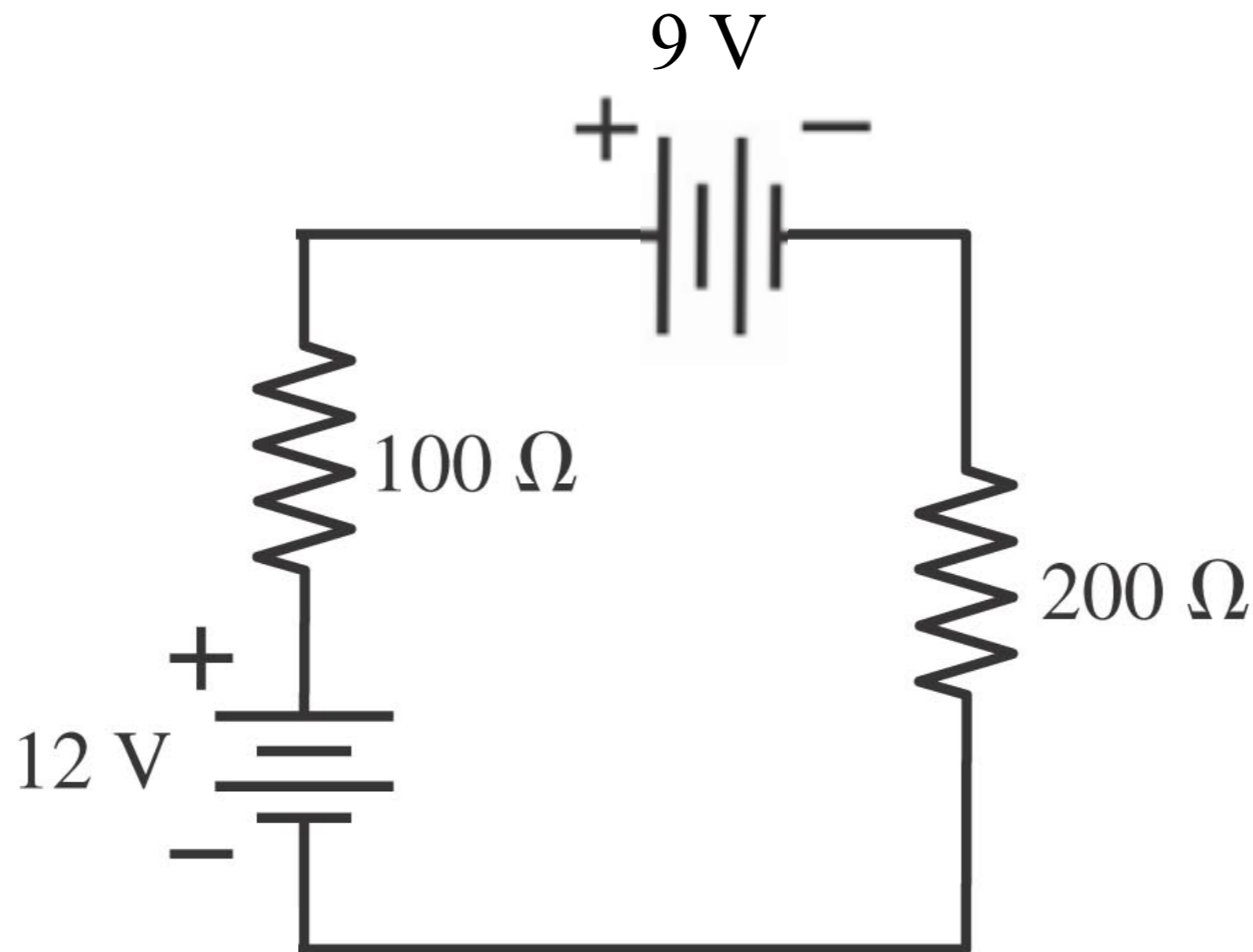
# The Loop Law in Action

Find the current running through the circuit.



# Clicker Question


Which light bulb is brighter?

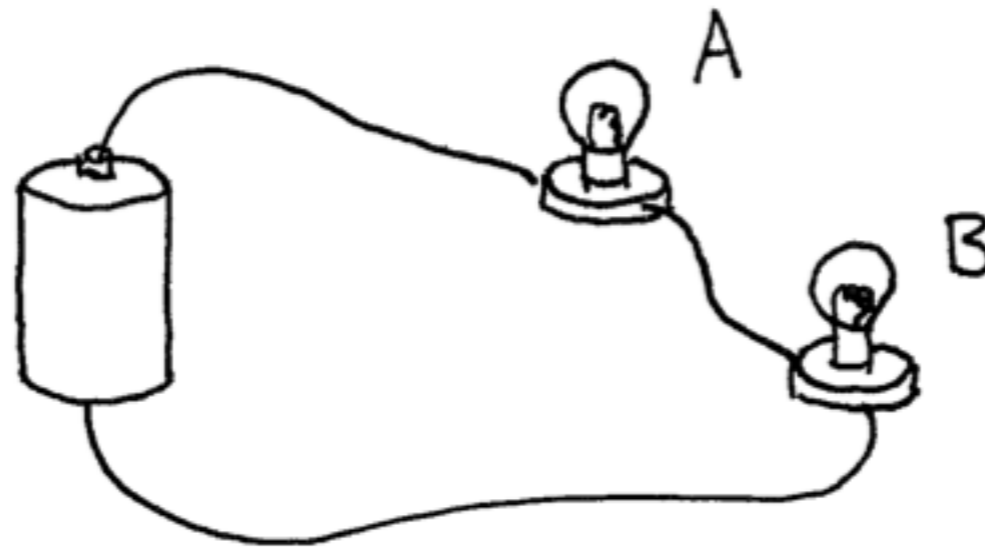

- a) A
- b) B
- c) both the same

# Clicker Question

Which light bulb is brighter?

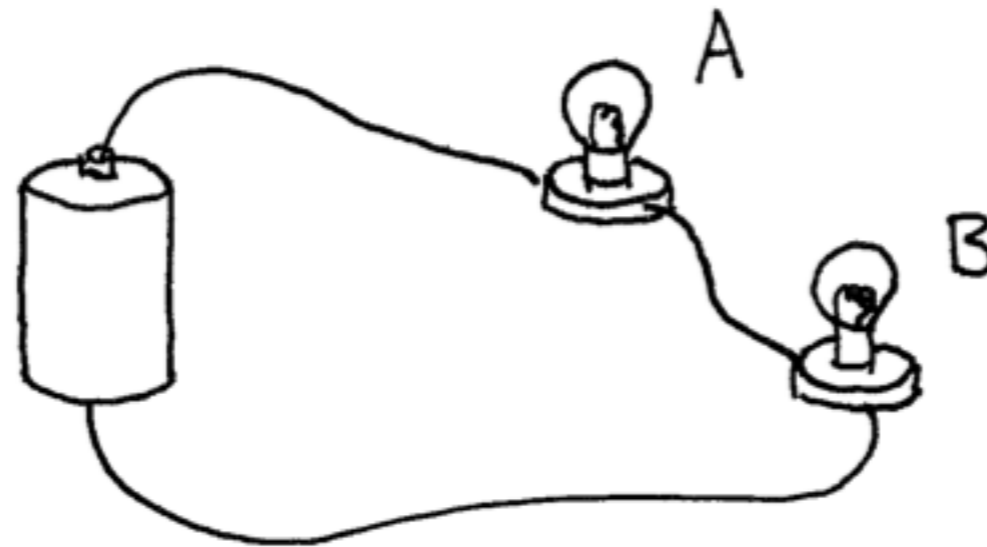


a) A

b) B

c) both the same

# Clicker Question


Which lightbulbs are brighter?

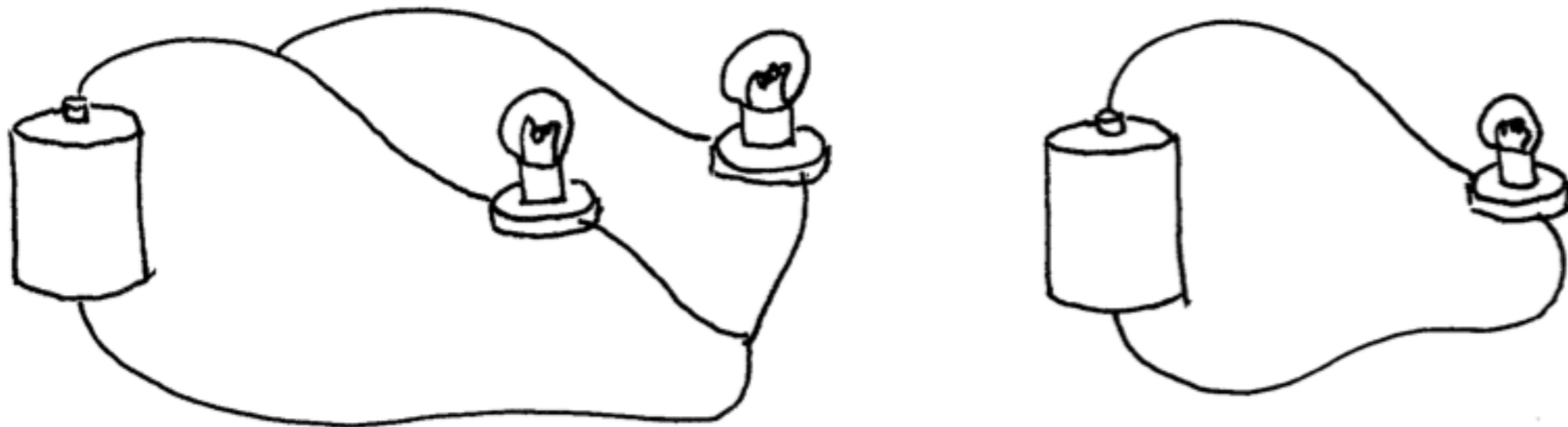

- a) the bulbs in the circuit on the left
- b) the bulb in the circuit on the right
- c) the left circuit has one bulb brighter and one bulb dimmer than the bulb in the right circuit.
- d) they're all the same brightness

# Clicker Question

Which lightbulbs are brighter?

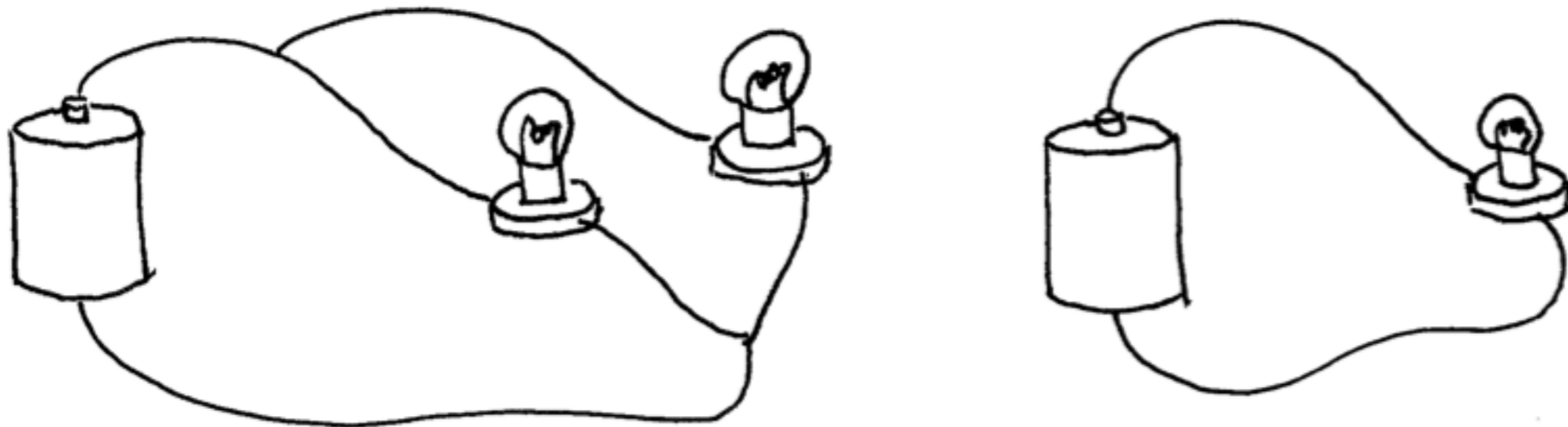


- a) the bulbs in the circuit on the left
- b) the bulb in the circuit on the right
- c) the left circuit has one bulb brighter and one bulb dimmer than the bulb in the right circuit.
- d) they're all the same brightness



**Circuits Galore**  
**Problems 3 and 4**
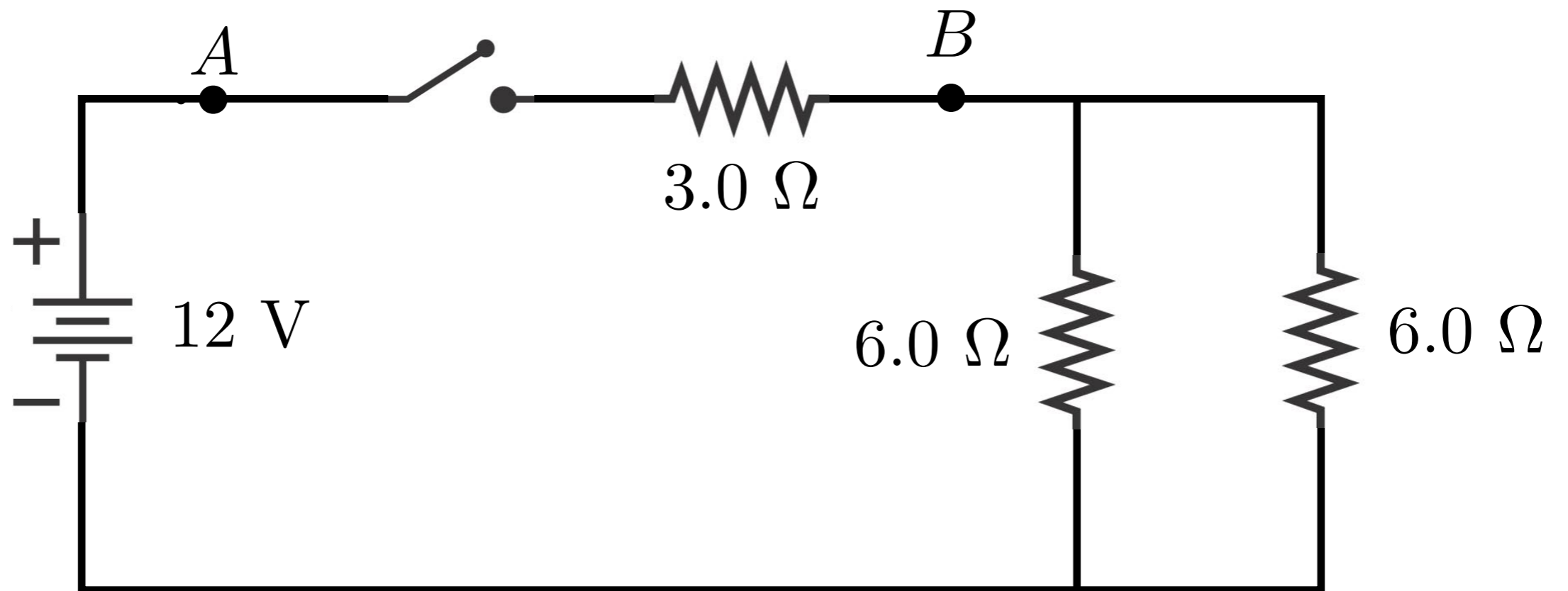
# Clicker Question


The switch is open. What is the potential difference between point *A* and *B*?



- a) 0 V
- b) 3 V
- c) 6 V
- d) 9 V
- e) 12 V
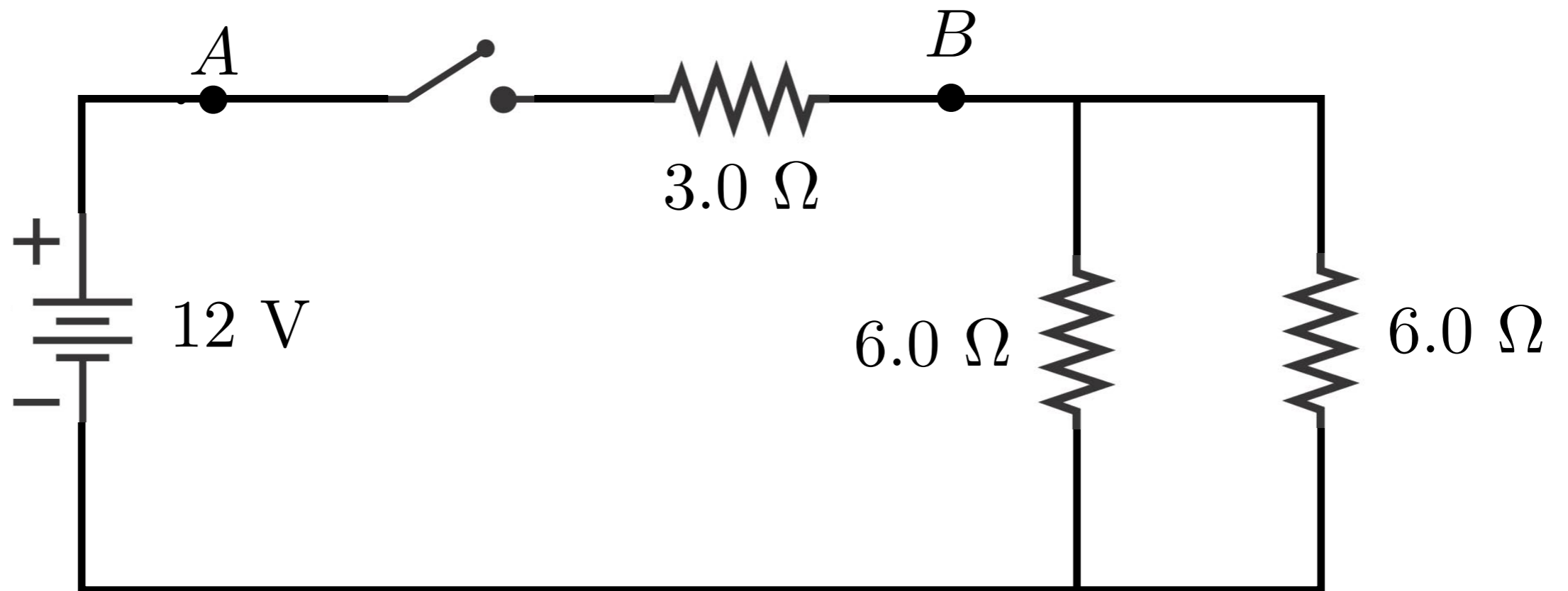
# Clicker Question

The switch is open. What is the potential difference between point *A* and *B*?




- a) 0 V
- b) 3 V
- c) 6 V
- d) 9 V
- e) 12 V

**Circuits Galore**  
**Problems 5, 6 and 7**
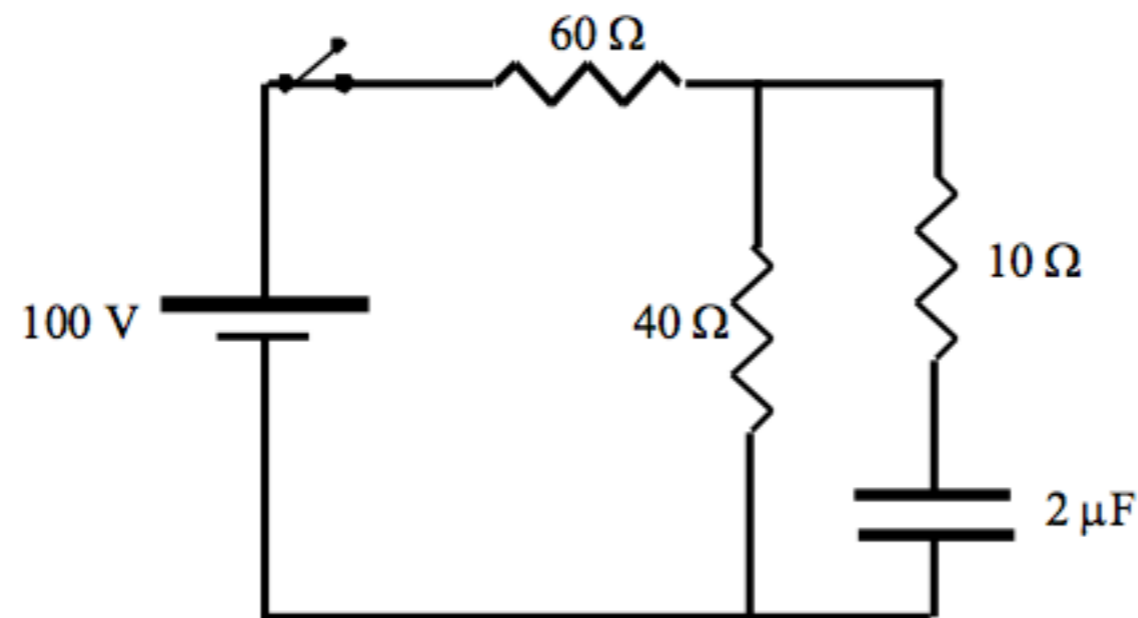
# Clicker Question


We close the switch. What is the voltage across the capacitor once the circuit has run for a while?



- a) 0 V
- b) 11.8 V
- c) 40 V
- d) 60 V
- e) Unable to determine.
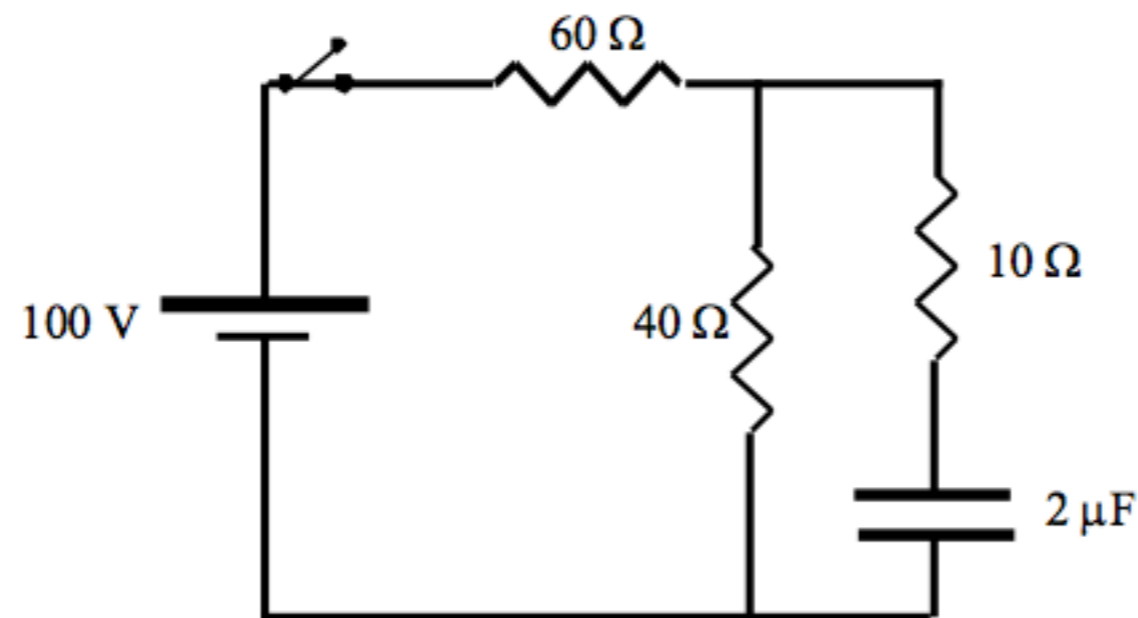
# Clicker Question


We close the switch. What is the voltage across the capacitor once the circuit has run for a while?



- a) 0 V
- b) 11.8 V
- c) 40 V**
- d) 60 V
- e) Unable to determine.

# RC Circuits

## Charging and Discharging Capacitors

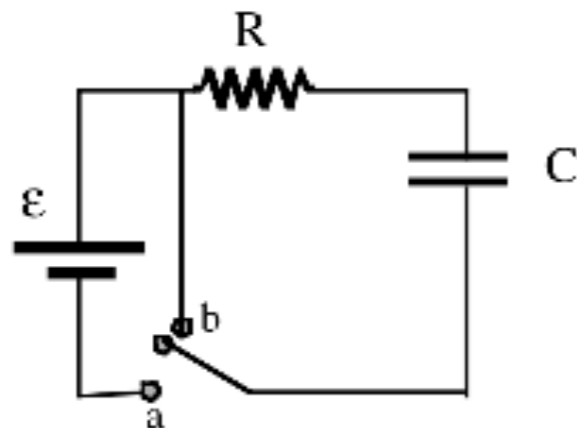

$$\begin{aligned} \epsilon &= 100 \text{ V} \\ R &= 1000 \ \Omega \\ C &= 1000 \ \mu\text{F} \end{aligned}$$


Switch to a  $\Rightarrow$  charge  $\Rightarrow$  long time  $\Rightarrow$  switch to b  $\Rightarrow$  discharge

Quantity	max value	Charge		Discharge	
		$t = 0$	$t = \infty$	$t = 0$	$t = \infty$
$q$					
$\Delta V_C$					
$I$					
$\Delta V_R$					

# RC Circuits


Charging and discharging a capacitor is governed by exponential laws.

charging:

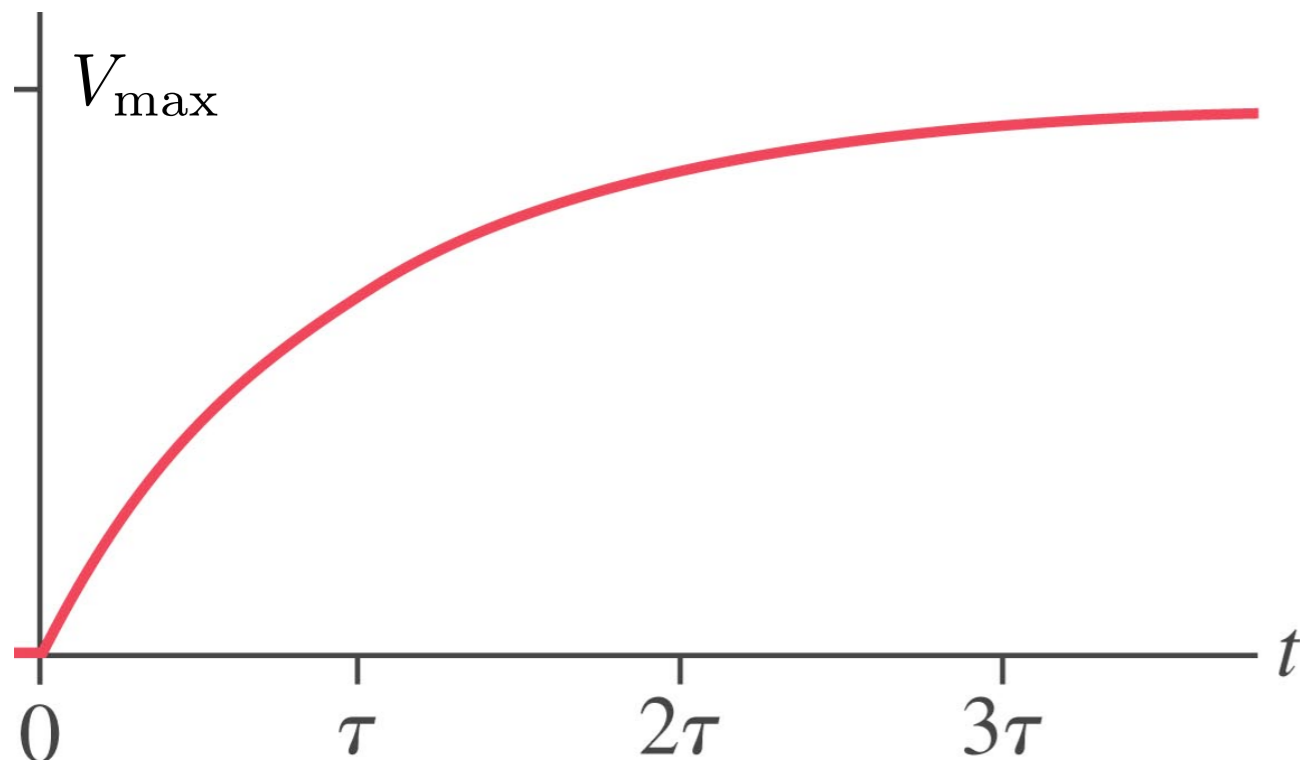

$$V_C = V_{\max} \left( 1 - e^{-t/RC} \right)$$

discharging:

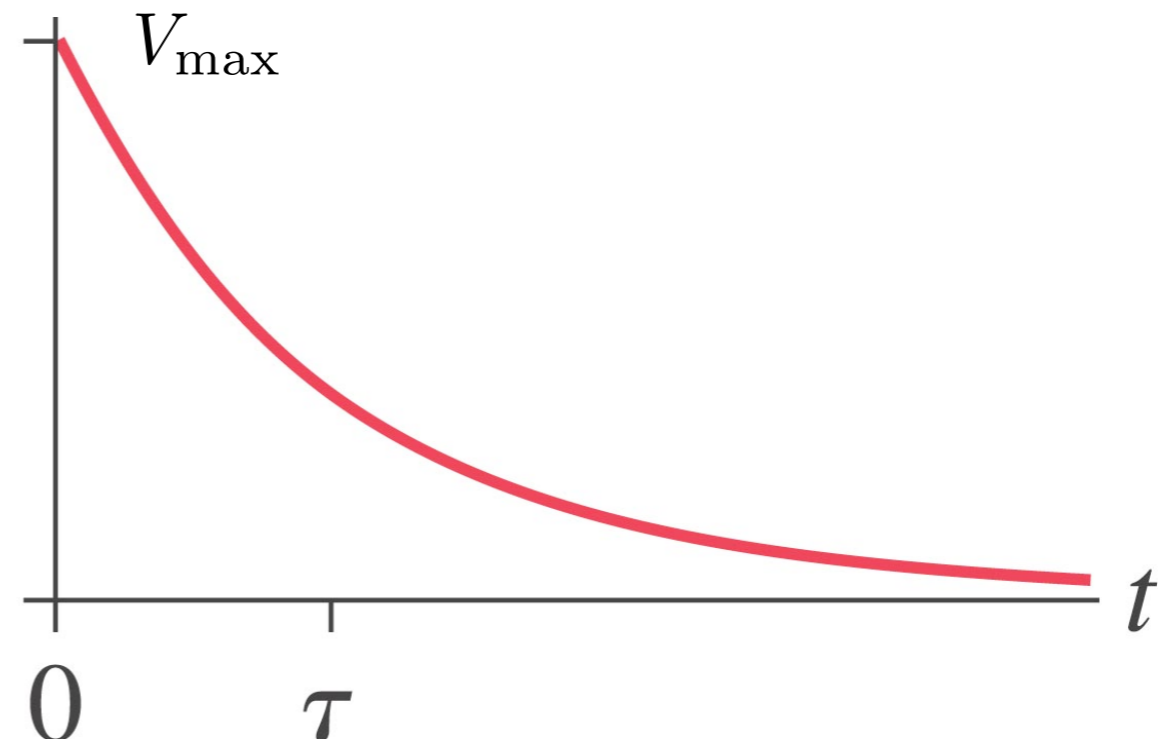

$$V_C = V_{\max} e^{-t/RC}$$




# RC Circuits

We can define a time constant to characterize the exponential decay

$$\tau = RC$$

It's mathematically identical to the lifetime in radioactive decay.

(b)

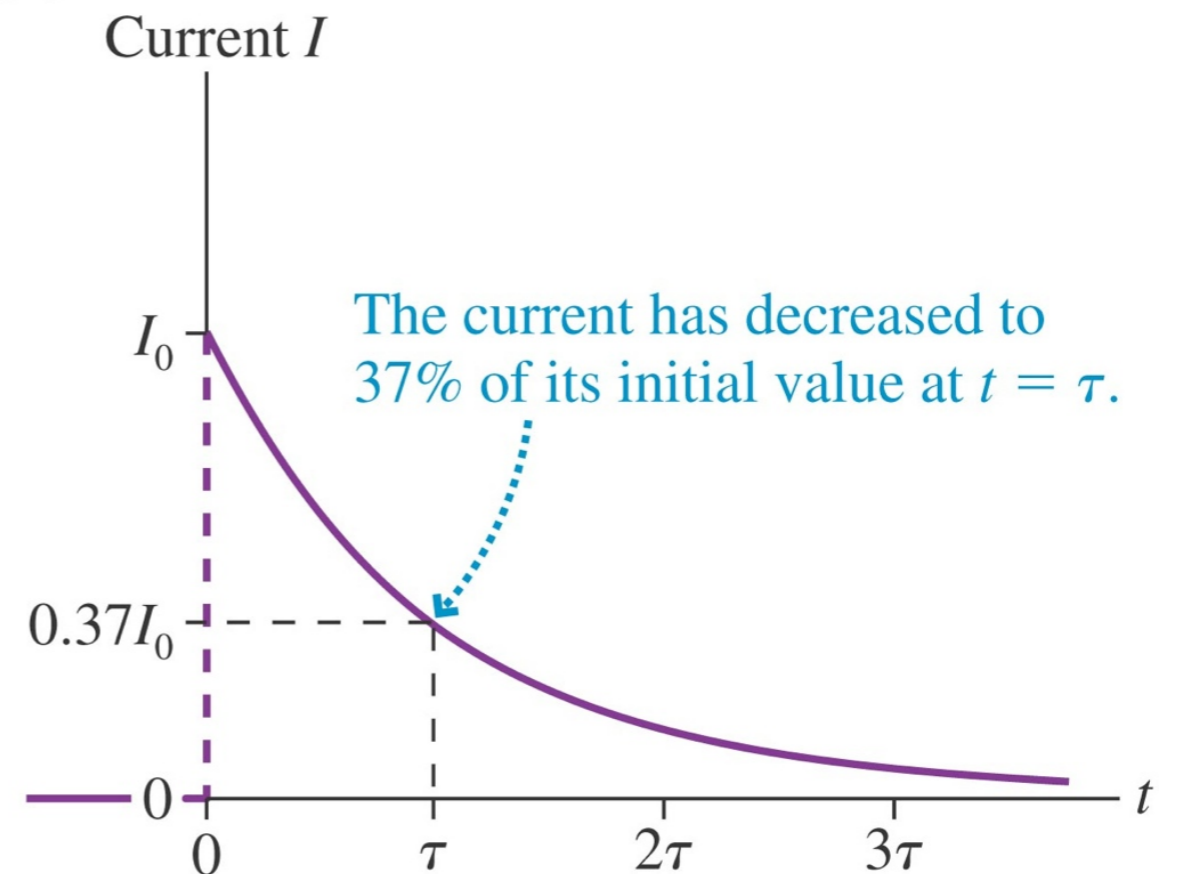


Copyright © 2008 Pearson Education, Inc., publishing as Pearson Addison-Wesley.

# Clicker Question

This graph shows  $V_C$  of a capacitor that is separately discharged through three different resistors.

Rank the value of the resistance from smallest to largest.

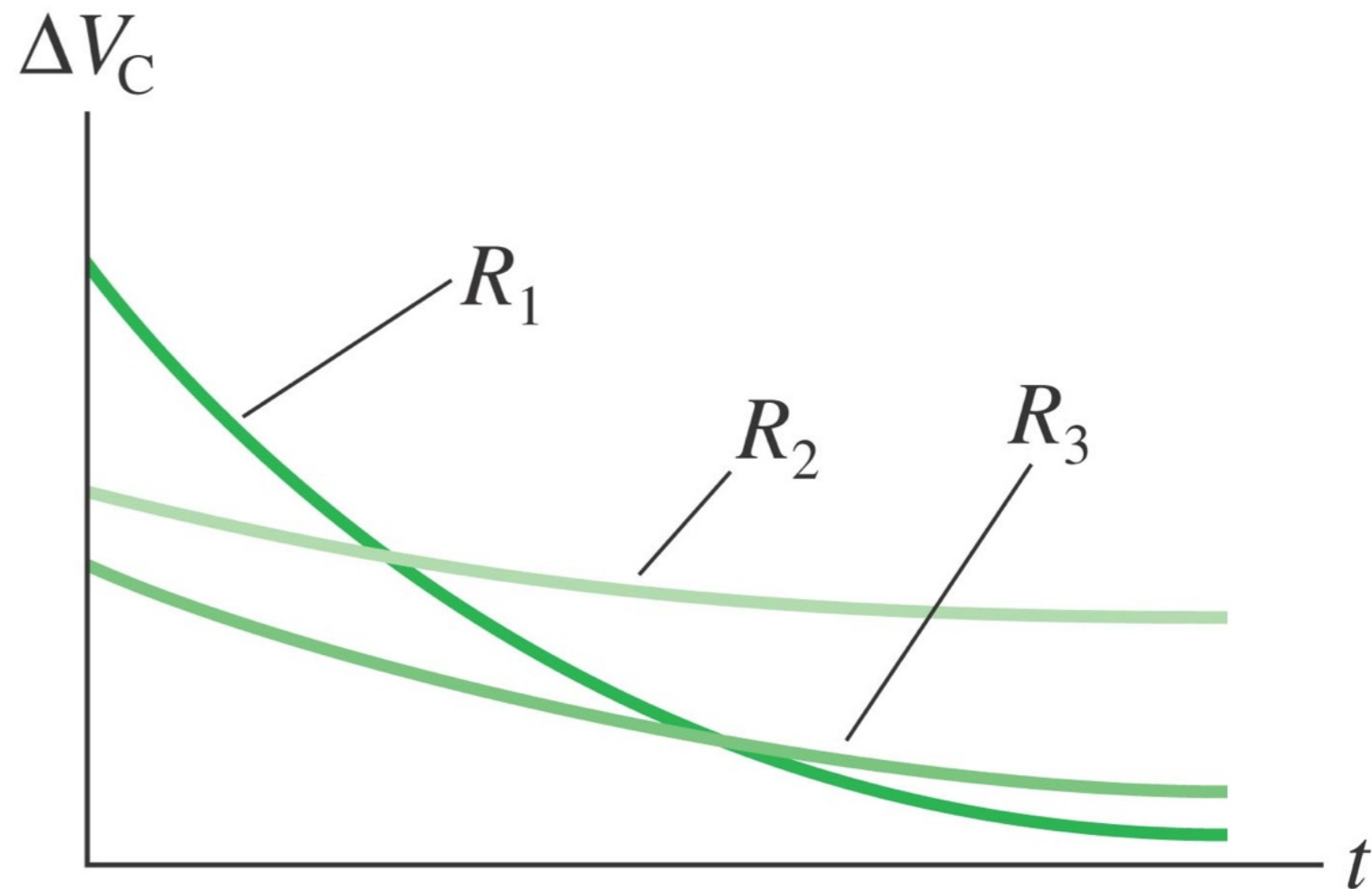- a)  $R_1 > R_2 > R_3$
- b)  $R_3 > R_2 > R_1$
- c)  $R_1 > R_3 > R_2$
- d)  $R_2 > R_3 > R_1$



# Clicker Question

This graph shows  $V_C$  of a capacitor that is separately discharged through three different resistors.

Rank the value of the resistance from smallest to largest.

- a)  $R_1 > R_2 > R_3$
- b)  $R_3 > R_2 > R_1$
- c)  $R_1 > R_3 > R_2$
- d)  $R_2 > R_3 > R_1$

