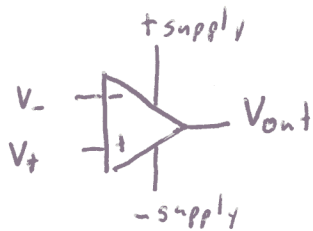


Op-amps

What is an Op-amp?




An integrated circuit amplifier built from transistors, resistors, capacitors and diodes

V_+ = non-inverting input
 V_- = inverting input

[LF 411 has 24 transistors
11 resistors
1 capacitor
4 diodes]

Properties

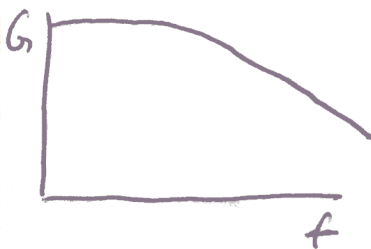- 1) Very high input impedance
- 2) Very high voltage gain [$G > 50,000$]
- 3) The op-amp attempts to make $V_{out} = G(V_+ - V_-)$
with the limitation: $V_{-supply} < V_{out} < V_{+supply}$
- 4) Gain depends on frequency:




The high gain is much too high for most applications. Op-amps are almost always used in circuits with feedback.

In such a circuit: Two "Golden Rules"

I) The op-amp "tries" to make $V_+ = V_-$

II) The inputs draw (almost) no current.

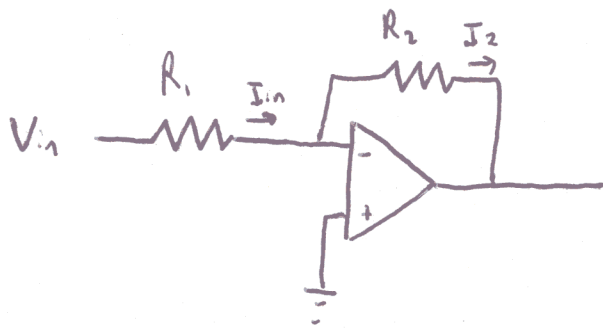

Questions:

- what is the gain of this circuit?
- what is the input impedance?
- what is the output impedance?

$$\text{Gain} = \frac{V_{out}}{V_{in}}$$

rule I says: $V_- = V_+$ so $V_- = 0$

rule II says: no current is drawn into the op-amp

$$\text{so } I_{in} = I_2$$

$$\frac{V_{in}}{R_1} = \frac{-V_{out}}{R_2}$$

$$\text{or } \boxed{\frac{V_{out}}{V_{in}} = \frac{-R_2}{R_1}}$$

We don't need to know the exact value of the open-loop gain!

To see how this works, imagine starting with $V_{in} = 0$, $V_{out} = 0$

Now increase V_{in} just a little. Current starts to flow through R_1 and R_2 (since no current flows into the amp). This raises

V_- above 0 so the op-amp swings its output down. V_{out} goes down until

$$G(V_+ - V_-) = V_{out}$$

If you don't want to believe in rule I:

$$\textcircled{1} \quad \frac{V_{in} - V_-}{R_1} = \frac{V_- - V_{out}}{R_2}$$

$$\textcircled{2} \quad -G_1 V_- = V_{out}$$

$$\textcircled{1} + \textcircled{2} \rightarrow \frac{V_{out}}{V_{in}} = -\frac{R_2}{R_1} \left[\frac{1}{1 + \frac{1 + R_2/R_1}{G_1}} \right]$$

as long as $G_1 \gg R_2/R_1$, then $\frac{V_{out}}{V_{in}} = -\frac{R_2}{R_1}$

so $V_- = -\frac{V_{out}}{G_1} \rightarrow$ always very close to 0.

V_- is called a virtual ground. It's not connected to ground, but the op-amp maintains its potential at very near ground.

Input impedance


$$Z_{in} \equiv \frac{V_{in}}{I_{in}}$$

$$\text{since } V_- \approx 0, \quad Z_{in} = \frac{V_{in}}{I_{in}} = R_1$$

Many signal sources demand a high input impedance amplifier!

Output impedance?

Model op-amp as:

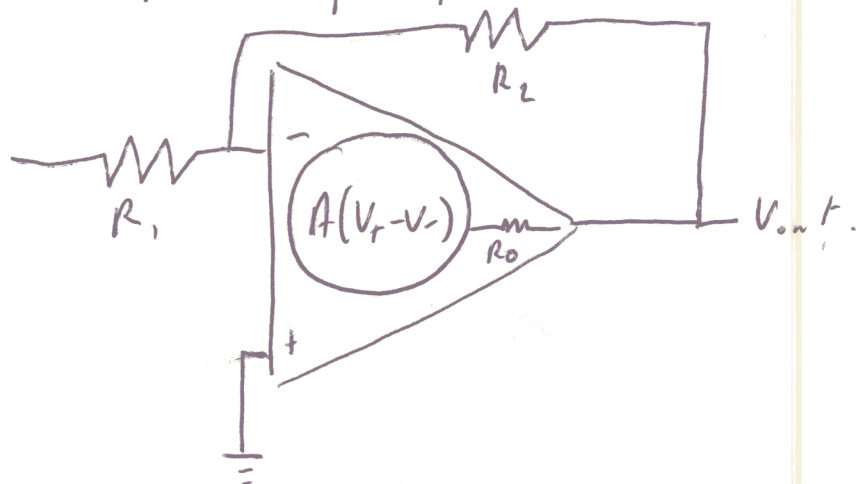

To calculate Z_{out} , short input to ground, then apply voltage V at the output terminal

then: $Z_{out} = \frac{V}{I_{out}}$

what is I_{out} ? $I_{out} = \frac{V_{out} - A(V_+ - V_-)}{R_o}$

if $V_{out} = V$, then $V_- = \frac{R_1}{R_1 + R_2} V$


so $I_{out} = \frac{V + A \frac{R_1}{R_1 + R_2} V}{R_o} = \frac{V}{R_o} \left(1 + \frac{A R_1}{R_1 + R_2} \right)$

$$Z_{out} = \frac{R_o}{1 + A \frac{R_1}{R_1 + R_2}}$$

Z_{out} is small!

Non inverting amplifier

(5)

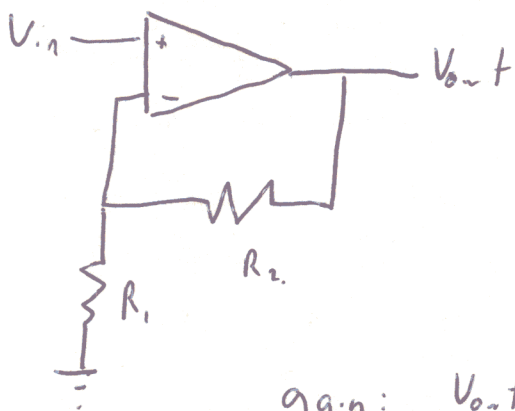

$$\text{gain: } \frac{V_{out} \times R_1}{R_1 + R_2} = V_{in}$$

$$\text{So } \frac{V_{out}}{V_{in}} = 1 + \frac{R_2}{R_1}$$


Input impedance: depends on op amp, typically $10^8 - 10^{12} \Omega$.

Output impedance: still less than 1Ω

Op amp Non-idealities.


- 1) Input offset current: rule II isn't quite true.
- 2) Open loop gain is frequency dependent.
- 3) Slew rate: max rate of change of V_{out}
- 4) Output current maximum
- 5) Offset voltage: with shorted inputs there is still an output voltage.

Other Op-amp applications

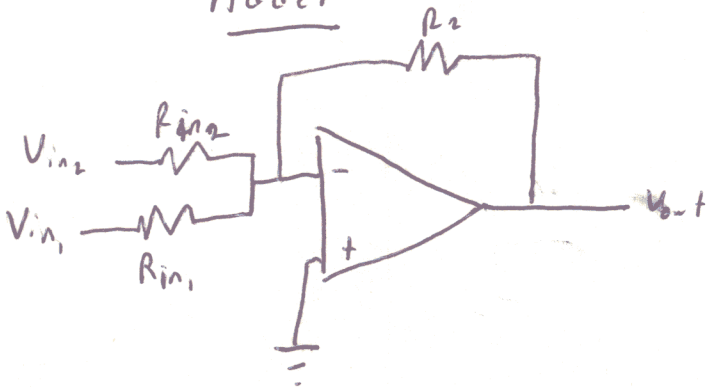Adder

$$V_{out} = \left(\frac{V_{in1}}{R_{in1}} + \frac{V_{in2}}{R_{in2}} \right) R_2$$


Follower:

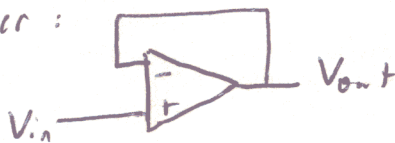

No voltage gain, but can have large current gain.

Multiply, divide (using diode to take ln or exp)


Integrate:

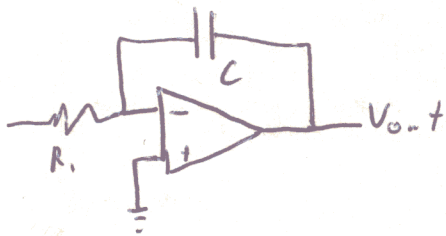

$$V_{out} = -\frac{1}{R_1 C} \int V_{in} dt$$

From: $V_- = 0$, $I_{in} = \frac{V_{in}}{R_1}$, $q = \int I_{in} dt$
and $V_{out} = -\frac{q}{C}$

Differentiate:

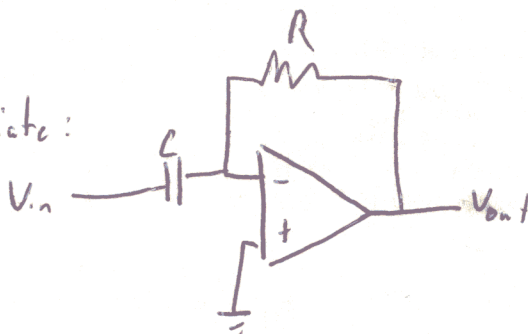

$$V_{out} = -RC \frac{dV_{in}}{dt}$$

From: $V_{out} = -IR = -R \frac{dq}{dt}$ and $V_{in} = \frac{q}{C}$