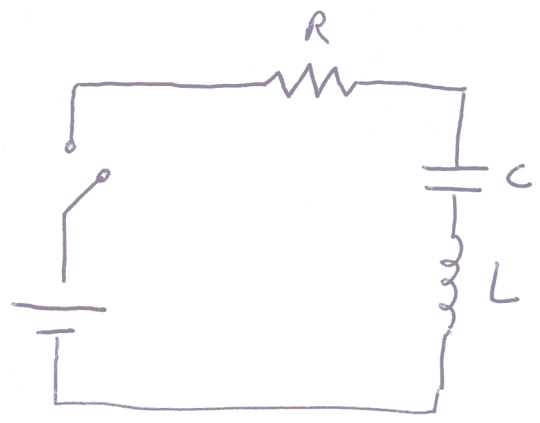


①

Transients in an RLC Series Circuit.



What happens when the switch is closed?

KVL: $V = iR + \frac{q}{C} + L \frac{di}{dt}$

differentiate:

① $0 = R \frac{di}{dt} + \frac{i}{C} + L \frac{d^2i}{dt^2}$

2nd order, linear d.e.

Look for solutions of the form:

$$i = e^{\lambda t}$$

$$\text{so } \frac{di}{dt} = \lambda e^{\lambda t}$$

$$\frac{d^2i}{dt^2} = \lambda^2 e^{\lambda t}$$

plug into ①:

$$0 = \lambda^2 + \frac{R}{L} \lambda + \frac{1}{LC} = 0$$

$$\lambda = \frac{-\frac{R}{L} \pm \sqrt{\left(\frac{R}{L}\right)^2 - \frac{4}{LC}}}{2}$$

define $\alpha = \frac{R}{2L}$ and $\omega_0^2 = \frac{1}{LC}$

(2)

$$\lambda_+ = -\alpha + \sqrt{\alpha^2 - \omega_0^2} \quad \lambda_- = -\alpha - \sqrt{\alpha^2 - \omega_0^2}$$

3 Cases

Case I: $\alpha^2 > \omega_0^2$ $\left[R^2 > \frac{4L}{C} \right]$ "Overdamped"

λ_+ and λ_- are both real #'s and are < 0

So our solution looks like

$$i(t) = A e^{\lambda_1 t} + B e^{\lambda_2 t}$$

To determine A and B we need two initial conditions.

$$i(0) = 0 \quad \left[\text{otherwise } \frac{di}{dt} \Big|_{t=0} = \infty \right]$$

get $i'(0)$ from KVL:

$$V = iR + \frac{q}{C} + L \frac{di}{dt}$$

$$\rightarrow \frac{di}{dt} \Big|_{t=0} = \frac{V}{L}$$

so

$$0 = A + B$$

$$\frac{V}{L} = A\lambda_1 + B\lambda_2$$

\Rightarrow

$$A = \frac{V}{L(\lambda_1 - \lambda_2)} = -B$$



Case II: $\alpha^2 = \omega_0^2$ "critically damped"

(3)

so $\lambda = -\alpha$

$$R^2 = \frac{4L}{C}$$

But now we have only 1 solution. Our second order d.e. must have 2 solutions.

Try: $i = f(t)e^{-\alpha t}$, plug into ①

find: $f''(t) = 0$

so $i = (A+Bt)e^{-\alpha t}$



Case III $\alpha^2 < \omega_0^2$ "under-damped"


$$\lambda = -\alpha \pm j\sqrt{\omega_0^2 - \alpha^2}$$

so $i(t) = Ae^{-\alpha t} \sin \omega t + Be^{-\alpha t} \cos \omega t$ where $\omega = \sqrt{\omega_0^2 - \alpha^2}$

using the initial conditions we find $B=0$

and $A = \frac{V}{\omega L}$

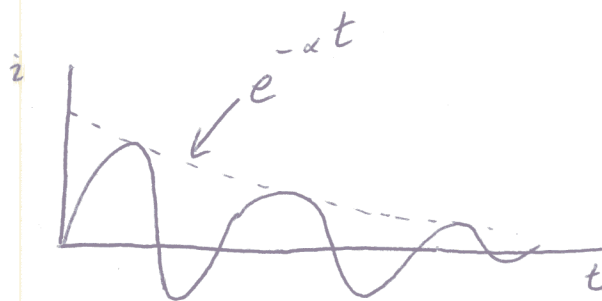so $i = \frac{V}{\omega L} \sin(\omega t) e^{-\alpha t}$



In the frequency domain, the bandwidth $\omega_2 - \omega_1 = \frac{R}{L} = 2\alpha$

ie the ring-down time constant $= \frac{2L}{R} \propto \frac{1}{\text{BW}}$